

# CMOS Power Factor Control IC

Masato Kashima  
Hironobu Shiroyama

## 1. Introduction

Most of the electronic systems in widespread use at present require rectifier circuits to convert alternating current into direct current as they utilize a DC power supply to drive their internal electronic circuits. Capacitor input filters are mainly used as the rectifier circuits. However, these have the undesired effect of producing a large amount of harmonic current due to the distorted input current waveform caused by the fact that the electric current flows into the input smoothing capacitor only when the alternating voltage is at a peak value. And at that time, the power factor drops to about 0.6. This type of increase in harmonic current may lead to malfunction of the electronic equipment, which may result in social problems. There is a movement to establish legal regulations for harmonic current problems. Increased loss in electric power transmission and distribution due to lowering of the power factor has also become problematic.

To resolve the problems of harmonic current and of lowered power factor, various measures have been proposed and active filters have come into widespread use as they are small and lightweight and can realize a high power factor.

As active filter control ICs, Fuji Electric had already commercialized power factor control ICs, FA5331P/M and FA5332P/M, which are based on average current mode control. This paper presents Fuji Electric's newly developed power factor control ICs, FA5500P/N and FA5501P/N, which are based on peak current mode control.

## 2. Overview of Power Factor Improving Circuit

Figure 1 shows a capacitor-input-rectifier circuit and its input voltage and current waveforms. The input current flows only during short intervals when the input voltage is in the vicinity of the peak voltage, and a large amount of harmonic current is generated. Existence of the harmonic current lowers the power factor, and the relation between them can be expressed by the following equations:

$$PF = 1/\sqrt{1 + THD^2}$$

$$THD = \sqrt{(i_2^2 + i_3^2 + \dots + i_n^2)/i_1^2}$$

Where,

PF: power factor,

THD: total harmonic distortion,

$i_1$ : input current fundamental harmonic,

$i_n$ :  $n$ -th order harmonic.

From these equations it is seen that the input harmonic current can be suppressed if the power factor can be improved by a power factor improving circuit.

Power factor is defined as the difference in phases between the waveforms of voltage and current. Accordingly, the power factor can be improved if the current waveform is controlled to be in-phase with that of the voltage. If phases of the voltage and current waveforms coincide completely, the power factor becomes 1.

Figure 2 shows a boost converter circuit used as an active filter circuit to control the current waveform. This is a boost converter circuit connected to a full wave rectifier circuit configured from a diode bridge. Switching element M1 of the circuit in Fig. 2 is switched on and off at a frequency substantially higher than that of the alternating voltage. And by control-

Fig.1 Capacitor-input-rectifier circuit and its input voltage and current waveforms

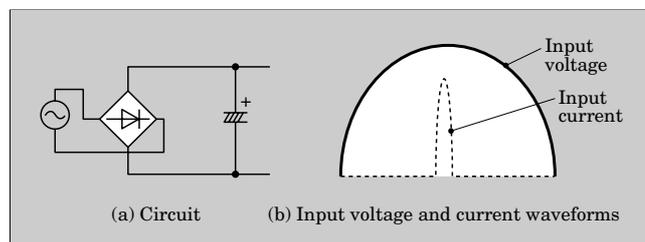


Fig.2 Boost converter circuit

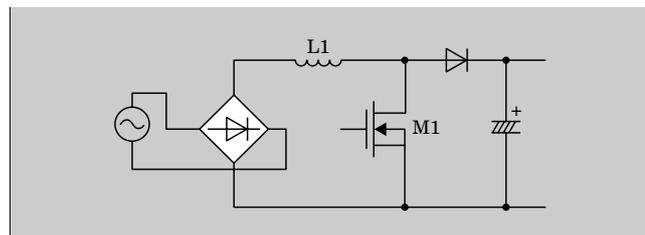




Fig.6 An example of typical application circuit


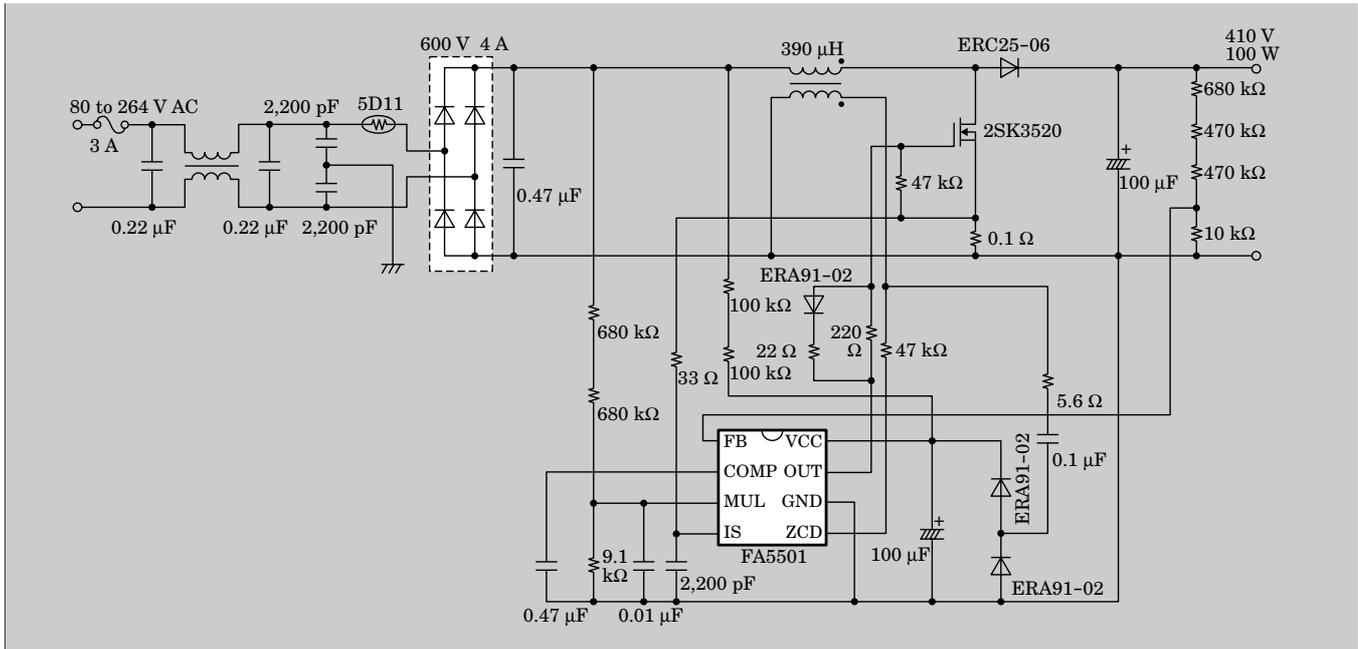


Fig.7 Waveforms of input voltage and current

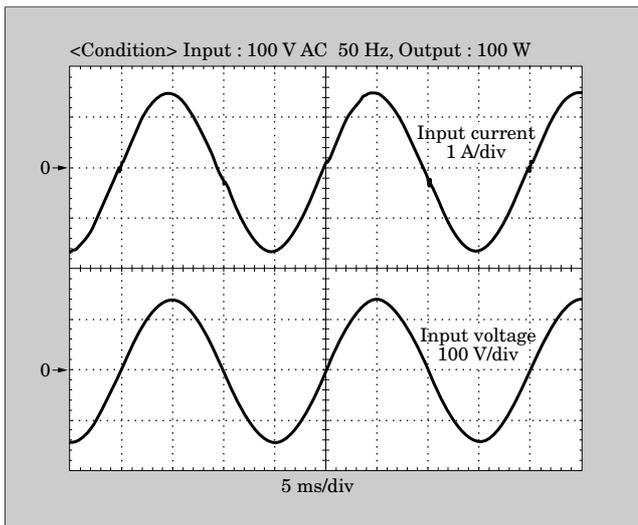

according to the on-voltage.

FA5500P/N: 11.5 V on / 9 V off

FA5501P/N: 13 V on / 9 V off

(6) Restart timer is built-in.

(7) Direct driving of power MOSFET (metal oxide semiconductor field effect transistor) is possible.

Output peak current: 500 mA source current and 1 A sink current

### 3.2 Correction circuit for light load

The power factor control circuit currently in use has a problem whereby the output voltage rises during light loads due to the influence of the internal circuit offset voltage of the power factor control IC.

As a countermeasure, the newly developed IC is equipped with an auto-offset control (AOC) circuit in

its internal current comparator to correct the offset voltage inside the IC. Thus, constant voltage control throughout the range from rated load to no-load has become possible by correcting the offset voltage in the internal circuit during light loads.

### 3.3 FB short detecting circuit

The IC is equipped with an FB short detecting circuit to stop the output from the IC in case the FB input becomes short-circuited to ground or becomes open-circuited. Accordingly, the external protection circuit that was required before can be omitted.

## 4. Typical Application

Figure 6 shows an active filter circuit with 100 W output as one of the typical applications of this IC. Figure 7 shows the waveforms of input voltage and current. The current waveform is sinusoidal and in-phase with the voltage waveform. It can be seen that the power factor is controlled to a value near 1 and that the current waveform has become sinusoidal by being averaged with the filter in the input stage.

## 5. Conclusion

An overview of the power factor control ICs that utilize peak current mode control has been presented. Demand for power factor improving circuits is expected to increase even more in the future. Fuji Electric intends to keep abreast of market needs by developing ICs with integrated power factor control circuitry and PWM (pulse width modulation) control circuitry to control DC output.



\* All brand names and product names in this journal might be trademarks or registered trademarks of their respective companies.